


Schematic using 8:1 MUX (4 points)

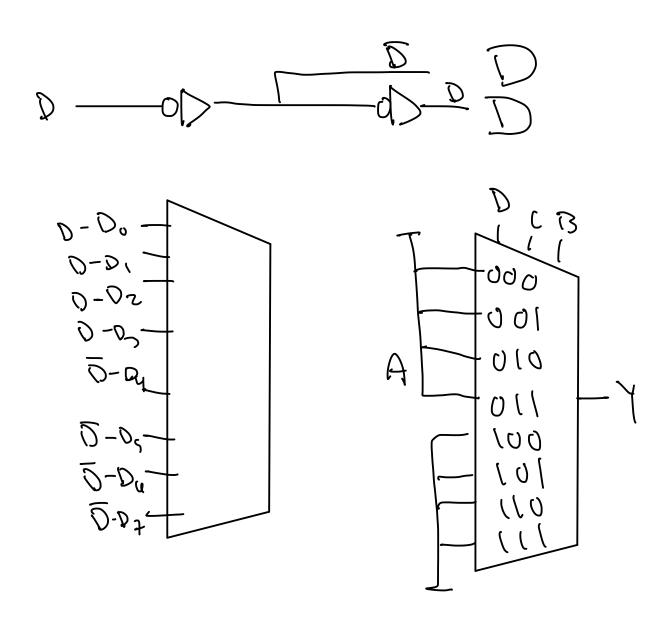

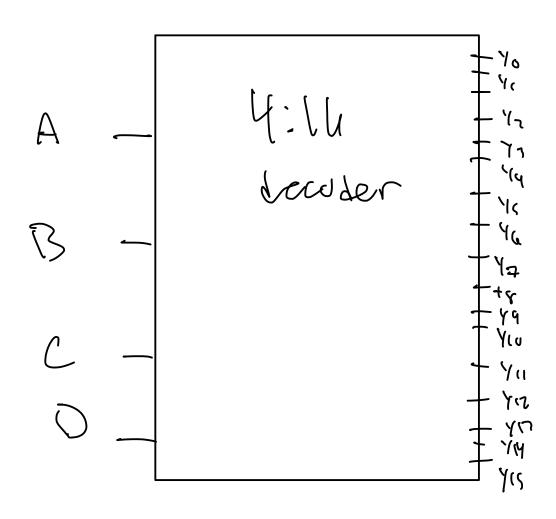Schematic using 4:16 one-cold decoder (4 points)



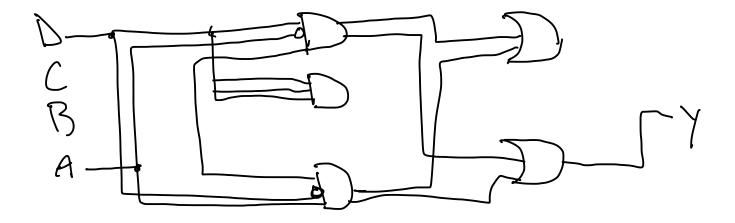Schematic using only NOT, OR, AND (4 points)



Schematic using NAND (3 points)

